



Basics of Digital Electronics (CE145)  
Tutorial - 2 (CE1 & CE2)

Q1 Draw NOT, AND, OR gate using

(a) only NAND & (b) only NOR gates.

Q2 write the truth table for the output  $f^n$  of following logic circuits

(a)

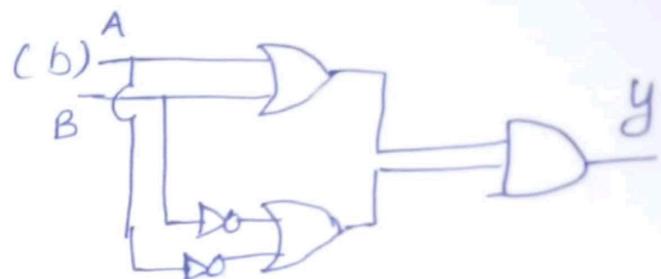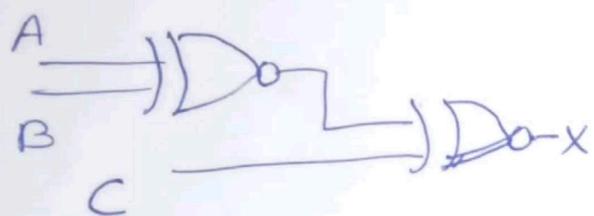

Q3 from the following Boolean function

draw the logic diagram

$$① y = AB + (\overline{A} + \overline{B})$$

$$② x = A + B + \overline{C}D$$

$$③ y = \overline{(AB)(\overline{A} + \overline{B})} + \overline{EF}$$

$$④ z = \overline{\overline{A}B} + \overline{CD} + ABC$$



$$⑤ A = y_1 \oplus y_2 (y_3 \odot y_4) + (y_5 \oplus y_6 \oplus y_7)$$

Tutorial 2



Q) Draw NOT, AND, OR using

- a) NAND gates.
- b) NOR gates.


NOT Gate :-

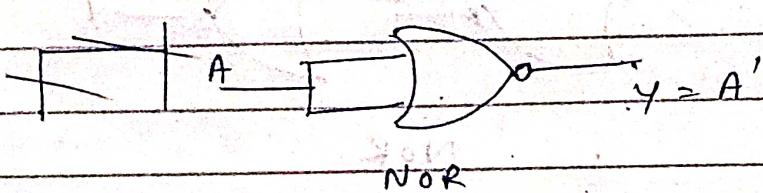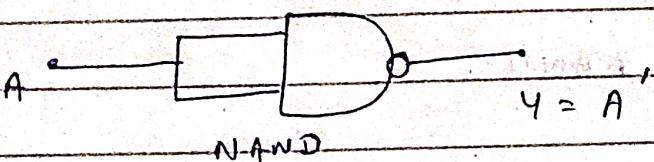


AND Gate :-

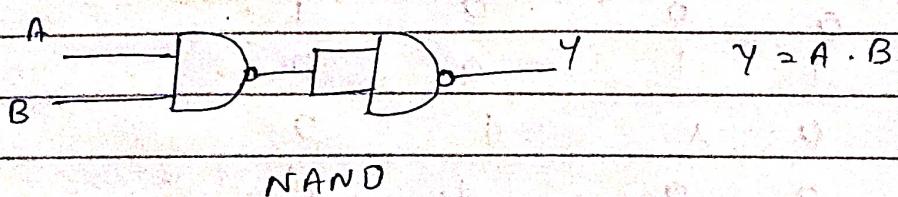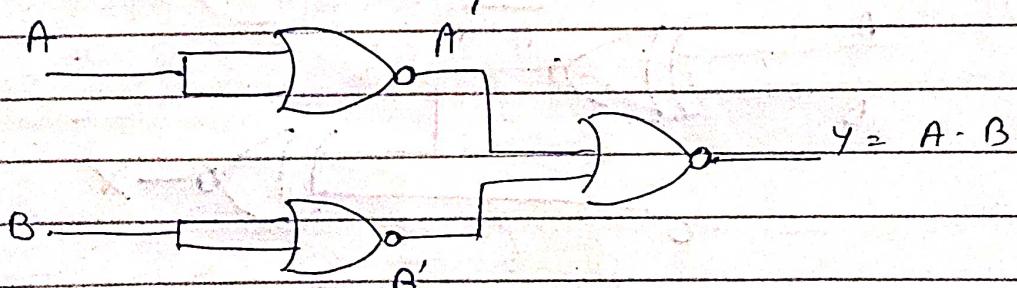

OR Create:

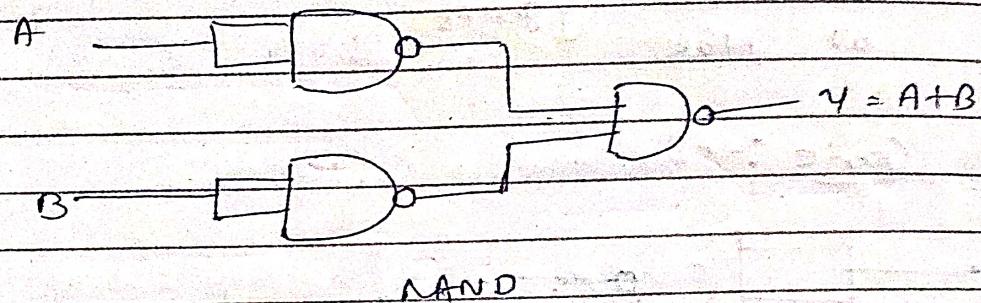


NAND

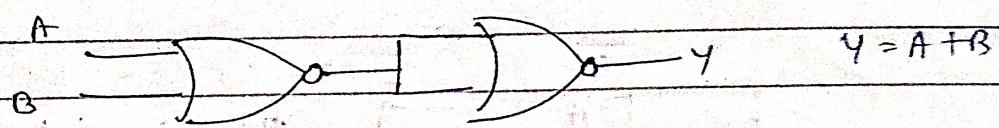

NOR


Q. a)

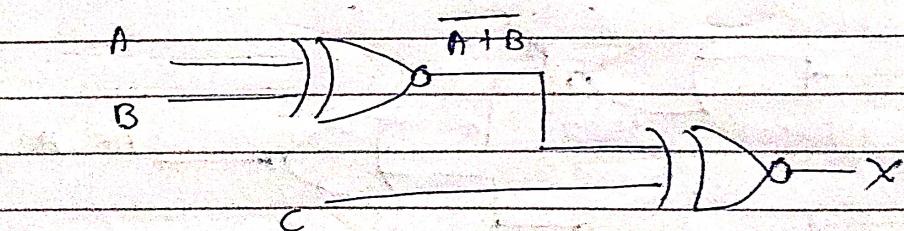

$$A \quad B \quad C \quad \overline{A+B} \quad X = \overline{\overline{A+B}+C}$$

A	B	C	$\overline{A+B}$	X
1	1	1	0	0
0	0	0	1	0
1	1	0	0	1
0	1	1	0	0
0	0	1	1	0
1	0	1	0	0
0	1	0	0	1
1	0	0	0	1


b)

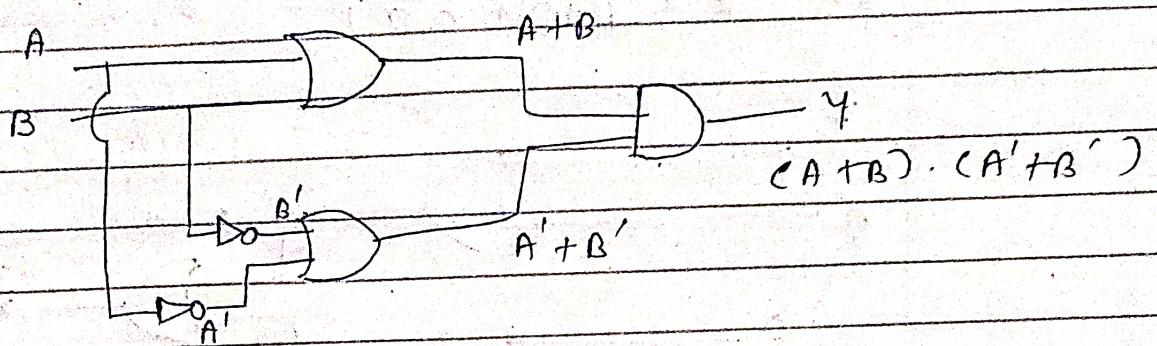


A	B	$A'$	$B'$	$A+B$	$A'+B'$	$y$
1	1	0	0	1	0	0
0	0	1	1	0	1	0
1	0	0	1	1	1	1
0	1	1	0	1	1	1

$$\textcircled{3} \text{. a)} \quad y = AB + CA\bar{B}$$


$$= AB + (\bar{A} \cdot \bar{B})$$

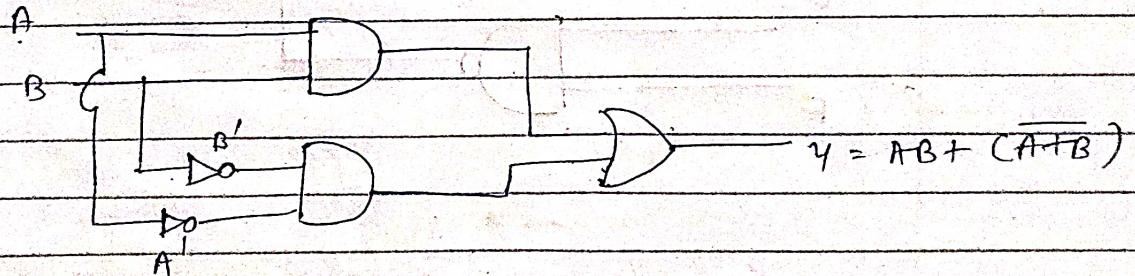

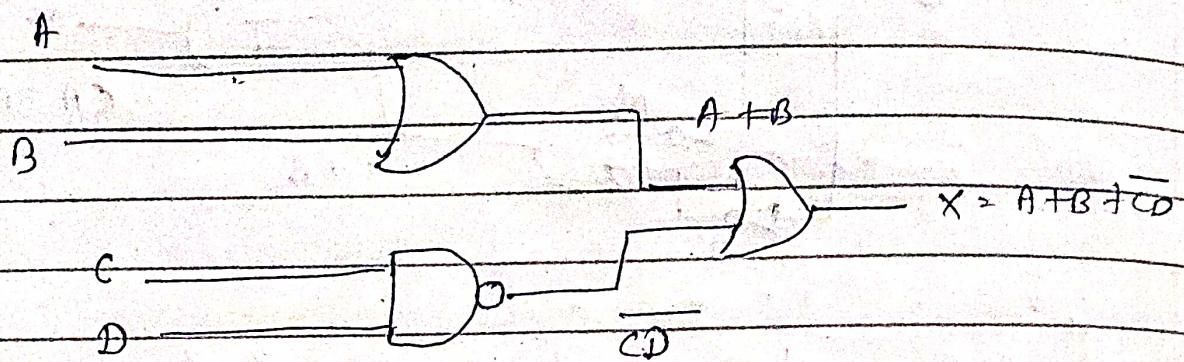
2)  $X = (A + B) \cdot (\overline{C} \cdot \overline{D})$



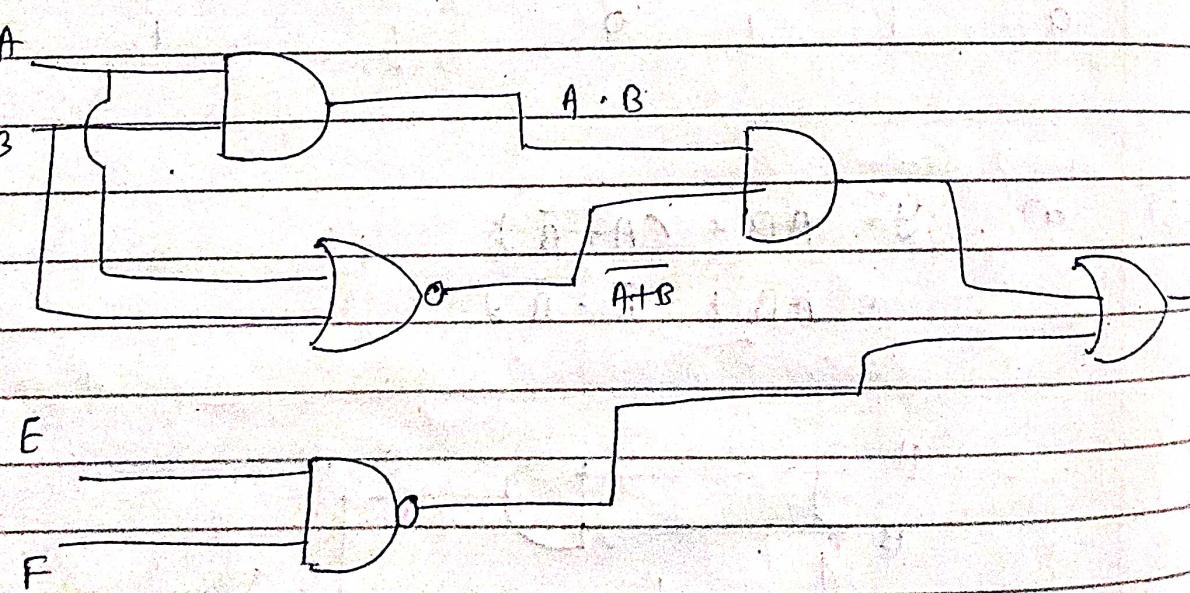3)  $y = (A \cdot B) \cdot (\overline{A} + \overline{B}) + \overline{E}F$



4)  $Z = \bar{A}B + C\bar{D} + ABC$

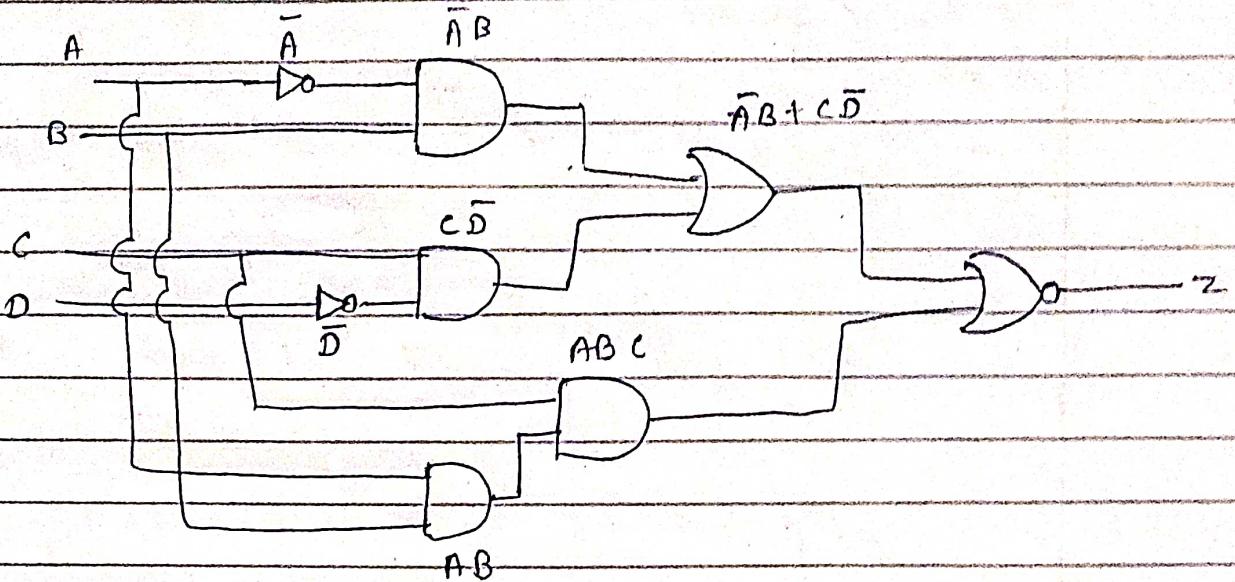

5)  $A = y_1 \oplus y_2 (y_3 \otimes y_4) + (y_5 \oplus y_6 \oplus y_7)$

